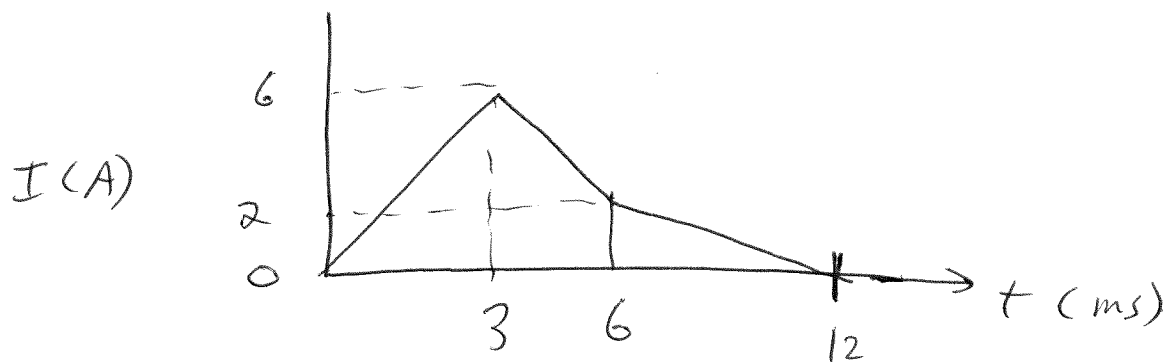


Ch. 14 Prob. 42

$$L = 5.0 \text{ mH}$$

$$R = 5.0 \Omega$$



$$\mathcal{E} = -L \frac{dI}{dt}$$

from  $t = 0 - 3 \text{ ms}$

$$\mathcal{E} = - (5.0 \times 10^{-3} \text{ H}) \left( \frac{6 \text{ A} - 0 \text{ A}}{3 \times 10^{-3} \text{ s} - 0} \right) = -10 \text{ V}$$

at  $t = \cancel{0} \cancel{.2} \text{ ms}$   $I = 4.0 \text{ A}$

so  $V = I \cdot R = (4.0 \text{ A})(5.0 \Omega) = 20 \text{ V}$

$\therefore V_{\text{tot}} = \mathcal{E} + V = -10 + 20 = \boxed{10 \text{ V}}$

from  $t = 3 - 6 \text{ ms}$

$$\mathcal{E} = - (5.0 \times 10^{-3} \text{ H}) \left( \frac{3 \text{ A} - 6 \text{ A}}{6 \times 10^{-3} \text{ s} - 3 \times 10^{-3} \text{ s}} \right) = \frac{3.00}{\cancel{6.00}} \text{ V}$$

at  $t = \cancel{3} \cancel{.0} \text{ ms}$   $I = 5.0 \text{ A}$

so  $V = I \cdot R = (5.0 \text{ A})(5.0 \Omega) = 25 \text{ V}$

$\therefore V_{\text{tot}} = \frac{3.00}{\cancel{6.00}} + 25 = \boxed{\cancel{3.00} \text{ V}} \boxed{28 \text{ V}}$

from  $t = 6 \text{ ms} - 12 \text{ ms}$

$$\mathcal{E} = - (5.0 \times 10^{-3} \text{ H}) \left( \frac{0 \text{ A} - 3 \text{ A}}{12 \times 10^{-3} \text{ s} - 6 \times 10^{-3} \text{ s}} \right) = \boxed{2.5 \text{ V}}$$

at  $t = \cancel{6} \cancel{.5} \text{ ms}$   $I = 2 \text{ A}$

so  $V = I \cdot R = (2 \text{ A})(5.0 \Omega) = 10 \text{ V}$

$\therefore V_{\text{tot}} = \cancel{2.5} \text{ V} + 10 \text{ V} = \boxed{12.5 \text{ V}}$