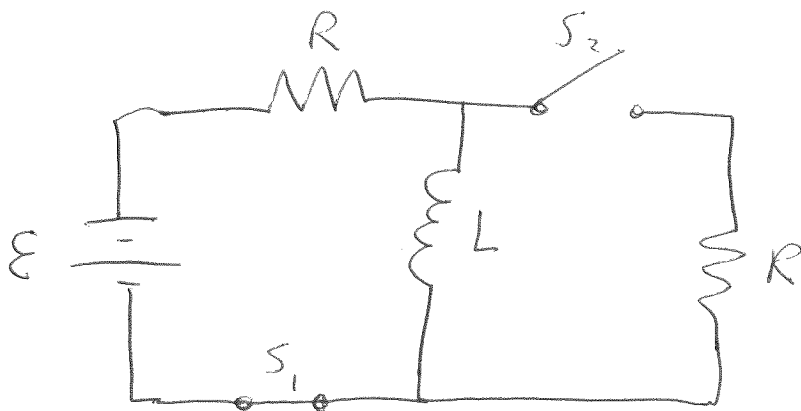


Ch. 14 Prob. 53

$\mathcal{E} = 20V$   
 $L = 4.0mH$   
 $R = 5.0\Omega$



At  $t=0$ ,  $S_1$  is opened +  $S_2$  is closed.

a) find current at  $t=0$

Model for the  $\frac{L}{R}$  circuit is  $I = I_0 e^{-t/\tau}$   
 where  $\tau = \frac{L}{R}$

$$I_0 = \frac{\mathcal{E}}{R} = \frac{20V}{5.0\Omega} = \boxed{4.0A}$$

b) Find the current at  $t = 4.0 \times 10^{-4}s$

$$\tau = \frac{L}{R} = \frac{4.0 \times 10^{-3}H}{5.0\Omega} = 8 \times 10^{-4}s$$

$$I = I_0 e^{-t/\tau} = (4.0A) e^{-\frac{4.0 \times 10^{-4}s}{8 \times 10^{-4}s}} = (4.0A) e^{-0.5} = \boxed{2.43A}$$

c) Find the voltage across  $L+R$  at  $t = 4.0 \times 10^{-4}s$

since  $I = 2.43A$ , Then  $V_R = I \cdot R = (2.43A)(5.0\Omega)$

By Kirchoff's Law the same voltage  $V_R = 12.15V$   
 with opposite sign must drop across  
 the inductor so

$V_L = 12.15V$   
 Textbook answer is wrong.