

Ch. 14 Prob. 62

$$C = 5000 \text{ pF} = 5.0 \times 10^{-9} \text{ F}$$

$$V = 100 \text{ V}$$

$$L = 80 \text{ mH} = 8.0 \times 10^{-2} \text{ H}$$

a) Find the max energy in the inductor.  
(magnetic)

Since all of the energy is in the capacitor

$$U_e = \frac{1}{2} CV^2 = \frac{(5.0 \times 10^{-9} \text{ F})(100 \text{ V})^2}{2} = 2.5 \times 10^{-5} \text{ J}$$

with no resistance, eventually all of this energy becomes magnetic energy in the inductor once the capacitor completely discharges.

$$\therefore U_m = 2.5 \times 10^{-5} \text{ J}$$

b) Find the peak value of current.

Since the energy is all inside the inductor

and  $U_m = \frac{1}{2} LI^2$ , then  $I = \sqrt{\frac{2U_m}{L}}$

$$I = \sqrt{\frac{2(2.5 \times 10^{-5} \text{ J})}{8.0 \times 10^{-2} \text{ H}}} = 0.025 \text{ A}$$

c) Find the frequency of the oscillation  
angular frequency of this circuit is

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(8.0 \times 10^{-2} \text{ H})(5.0 \times 10^{-9} \text{ F})}} = 5.0 \times 10^4 \frac{\text{rad}}{\text{s}}$$

Convert to Hertz gives

$$f = \frac{\omega}{2\pi} = \frac{5.0 \times 10^4 \frac{\text{rad}}{\text{s}}}{2\pi} = 7,960 \text{ Hz}$$